

## ECE322 Lab 5 –Peak Detector Circuits

### I. Introduction

In class we have discussed peak detectors circuits using the constant drop diode approximation. In this lab, we will analyze these structures and simulate their practical performance.

### II. Objectives

The objectives of this laboratory are to

1. Build and simulate the performance of the simple peak rectifier circuit.
2. Build and simulate the performance of the peak detector with superdiode.

### III. Motivation

Peak detectors (peak rectifiers) are designed into numerous applications ranging from AM demodulation to detecting signal presence or absence.

### IV. Materials

The materials for this laboratory will include the LTSpice simulator and models for the 1N4148 diode and LM324 opamp components and lab bench equipment and prototyping parts. Use opamp supplies of +/-10 Volts. Export data from LTSpice to overlay with the experimental data in EXCEL.

### V. Lab – Circuit Investigation

#### A. Simple peak detector

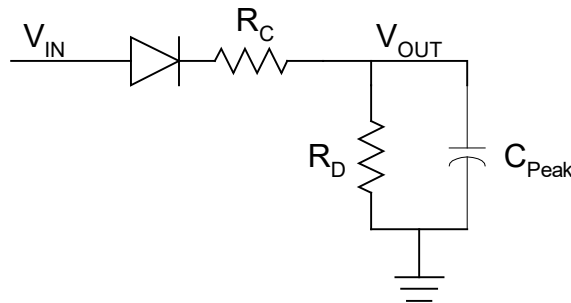


Figure 1. Peak Rectifier Circuit

For the circuit of Figure 1, run a Spice transient simulation with  $R_C=200$ ,  $R_D=100K$ , and  $C_{Peak}=0.1\mu F$ . Apply an input sin wave with *peak-to-peak* amplitude of 4Vpp at 1kHz. Run the transient for 5mS.

## B. Peak detector with superdiode structure analysis and simulation

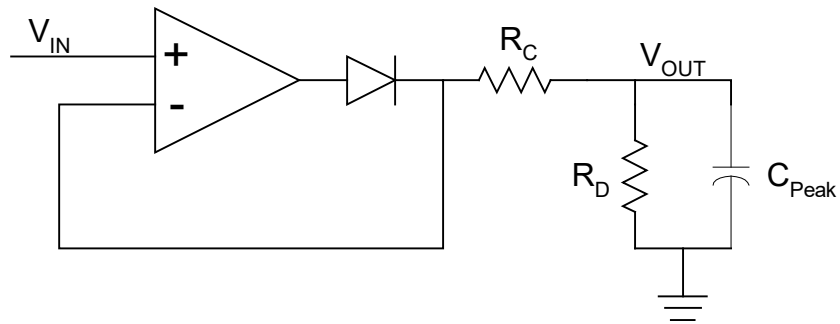


Figure 2. Peak Detector Circuit

For the circuit of Figure 2, perform a Spice transient simulation with  $R_C=200$ ,  $R_D=100K$ , and  $C_{Peak}=0.1\mu F$ . Apply an input sin wave with *peak-to-peak* amplitude of 4Vpp at 1kHz. Run the transient for 5mS. Use opamp supplies of +/-10Volts.

**VI. Summary**

Pull your lab together in a 2 page or less memo, overlaying experimental and simulation results and brief explanations of circuit operation.